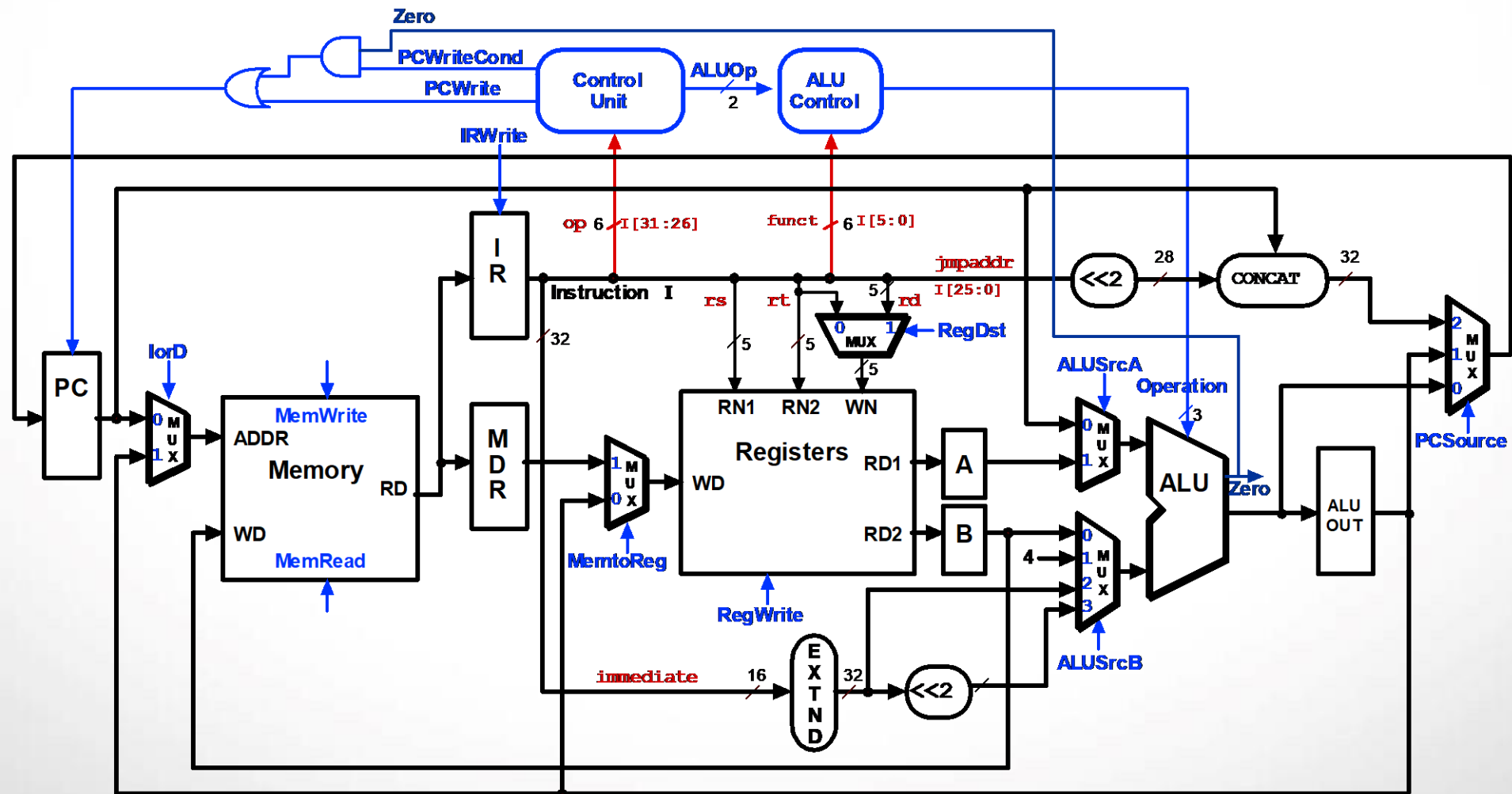


# 多周期执行步骤

- 指令执行 3 到 5 个时钟周期

Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	IR = Memory[PC] PC = PC + 4			
Instruction decode/register fetch	A = Reg [IR[25-21]] B = Reg [IR[20-16]] ALUOut = PC + (sign-extend (IR[15-0]) << 2)			
Execution, address computation, branch/jump completion	ALUOut = A op B	ALUOut = A + sign-extend (IR[15-0])	if (A ==B) then PC = ALUOut	PC = PC [31-28]    (IR[25-0]<<2)
Memory access or R-type completion	Reg [IR[15-11]] = ALUOut	Load: MDR = Memory[ALUOut] or Store: Memory [ALUOut] = B		
Memory read completion		Load: Reg[IR[20-16]] = MDR		


# 完整数据通路 & 控制



# 多周期执行步骤 (1) : R-Type

IR = Memory[PC];


PC = PC + 4;

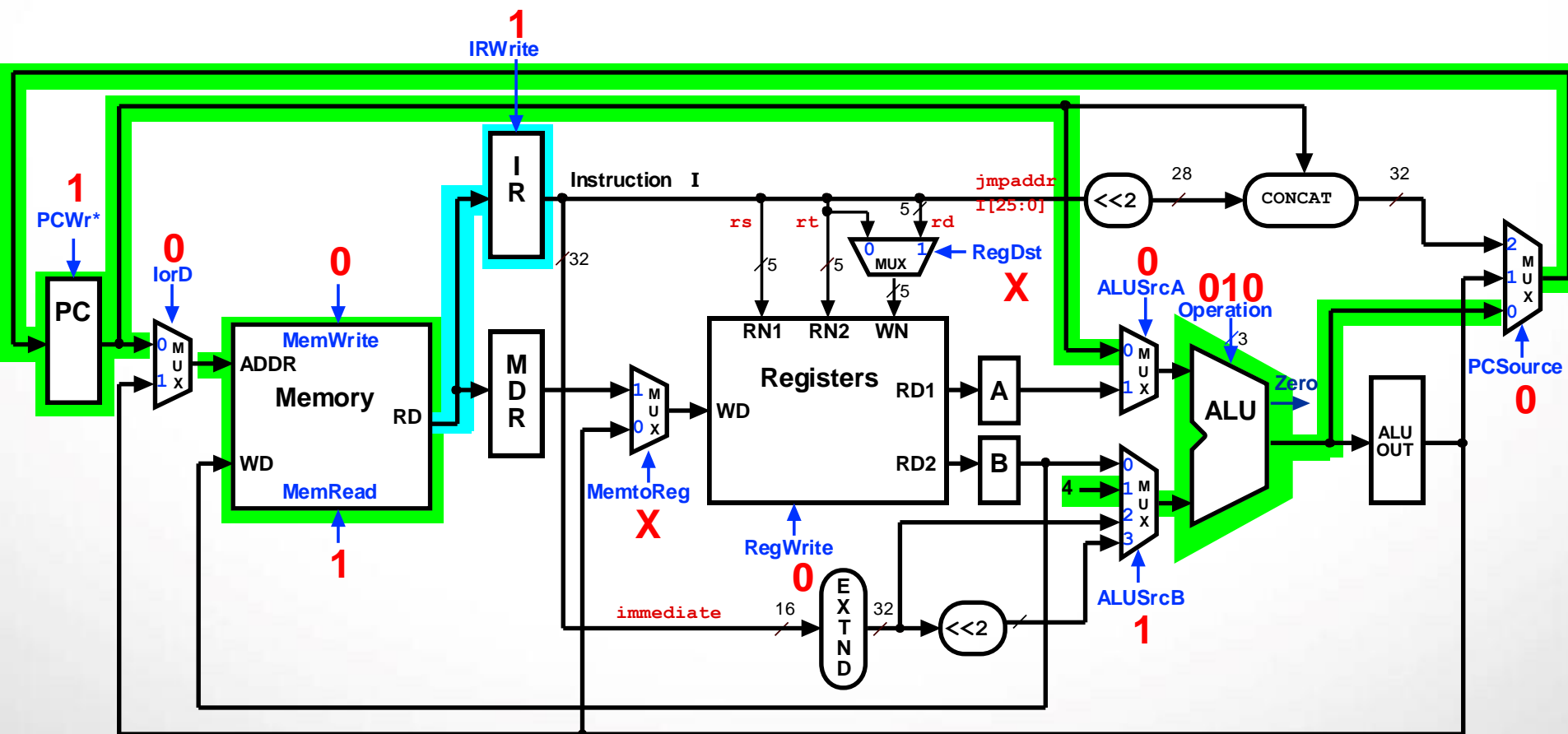
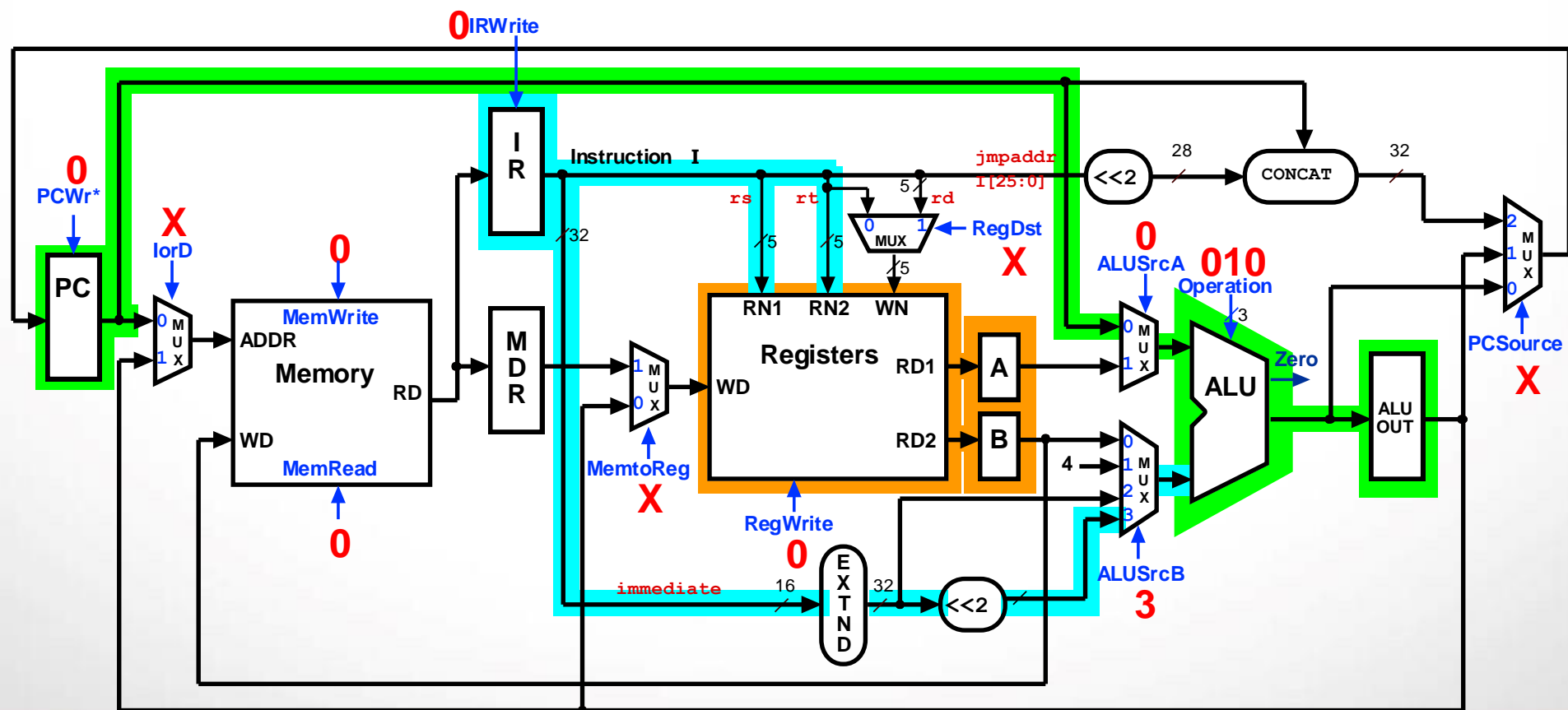
## 多周期执行步骤 (2) : R-Type


```

A = Reg[IR[25-21]];          (A = Reg[rs])
B = Reg[IR[20-15]];          (B = Reg[rt])
ALUOut = (PC + sign-extend(IR[15-0]) << 2)
    
```



# 多周期执行步骤 (3) : R-Type


ALUOut = A op B

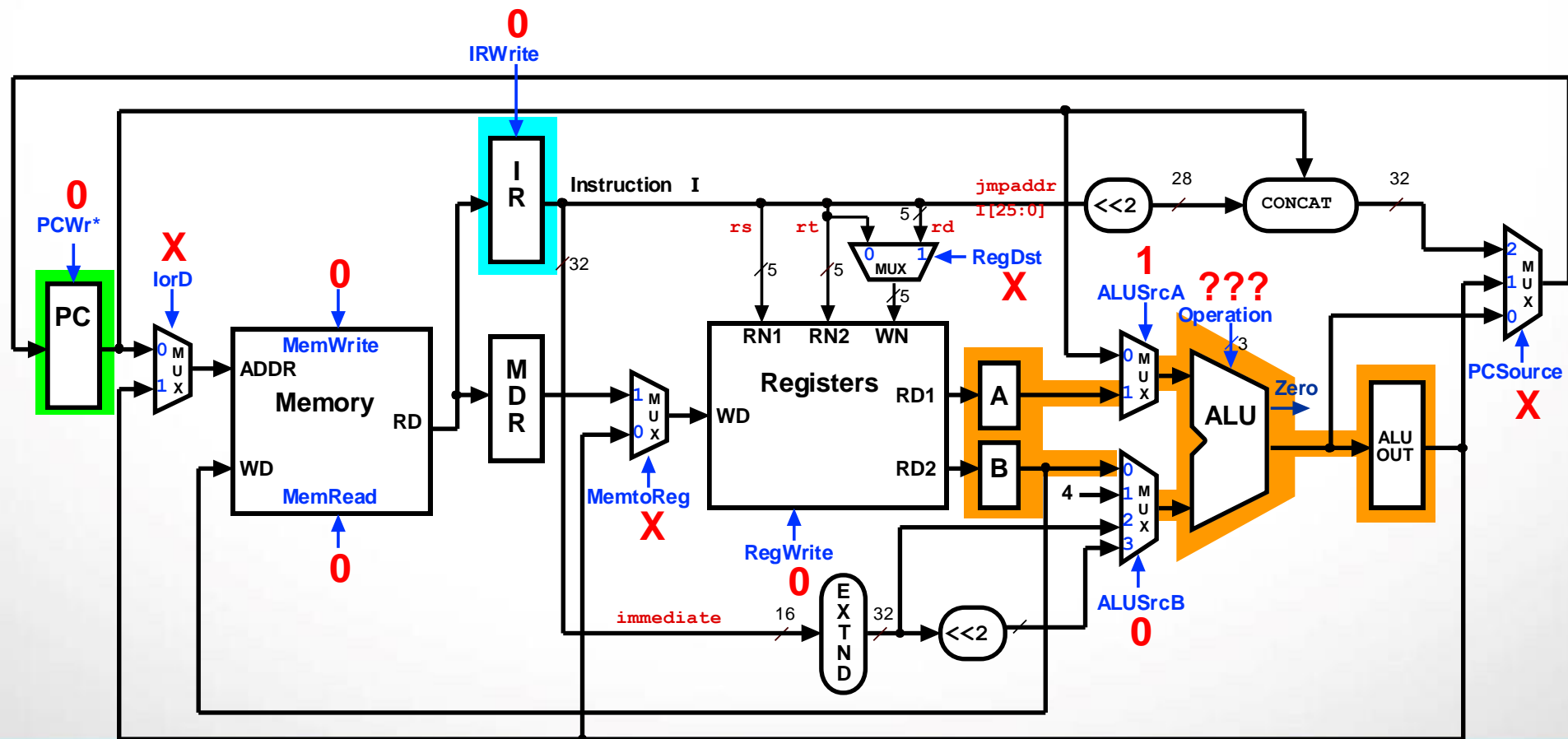
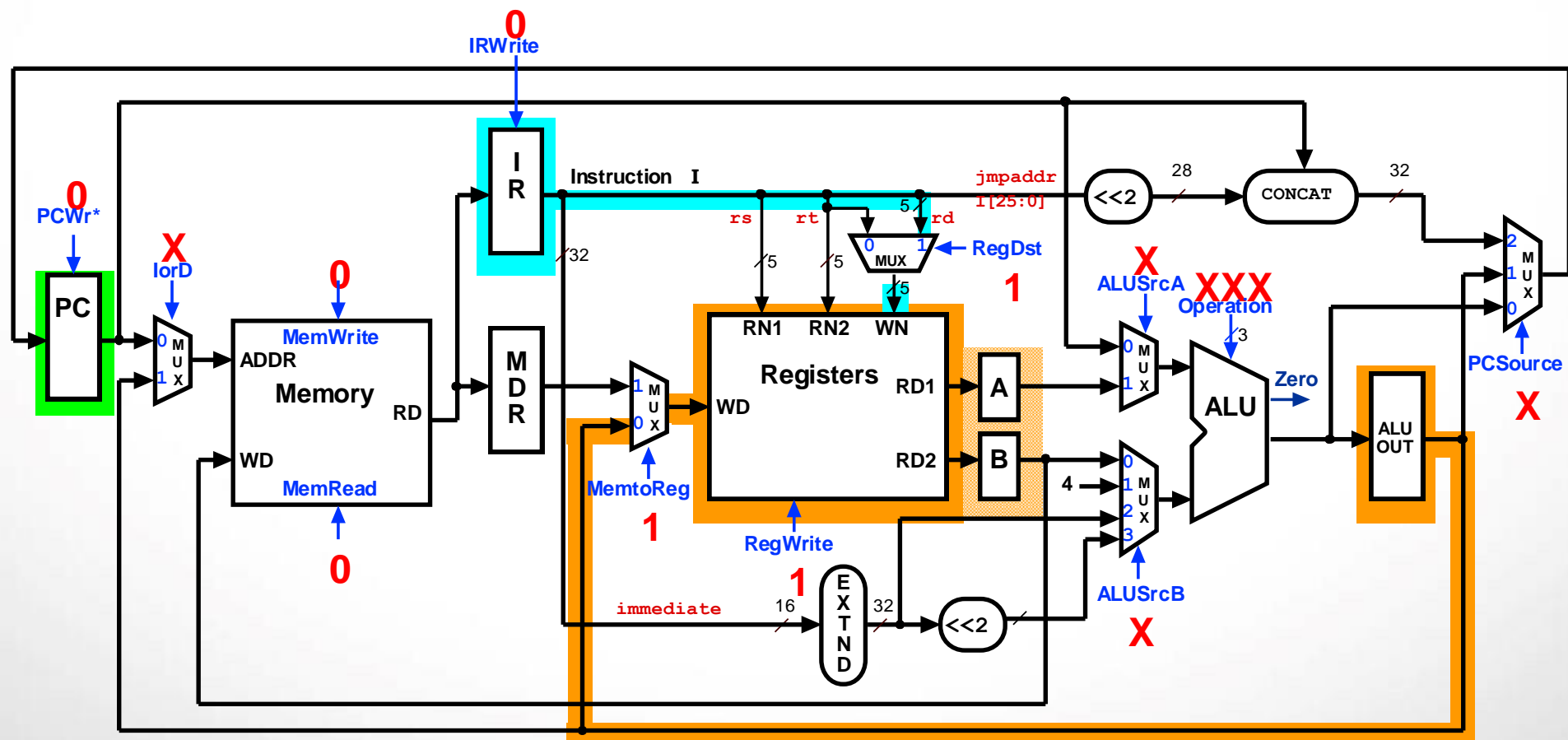
# 多周期执行步骤 (4) : R-Type

$\text{Reg}[\text{IR}[15:11]] = \text{ALUOut};$


$(\text{Reg}[\text{Rd}] = \text{ALUOut})$



# 多周期执行步骤 (1):lw

IR = Memory[PC];


PC = PC + 4;

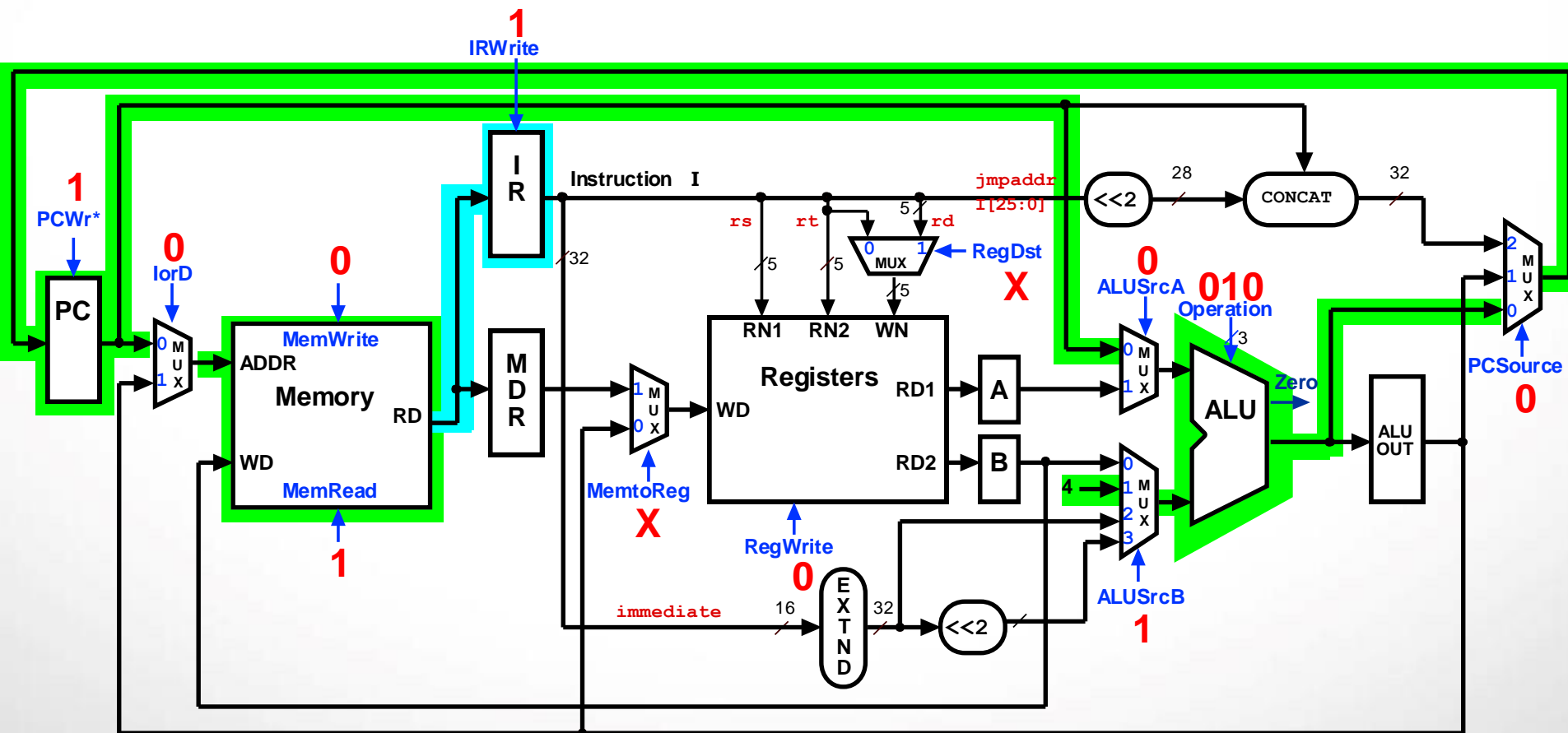
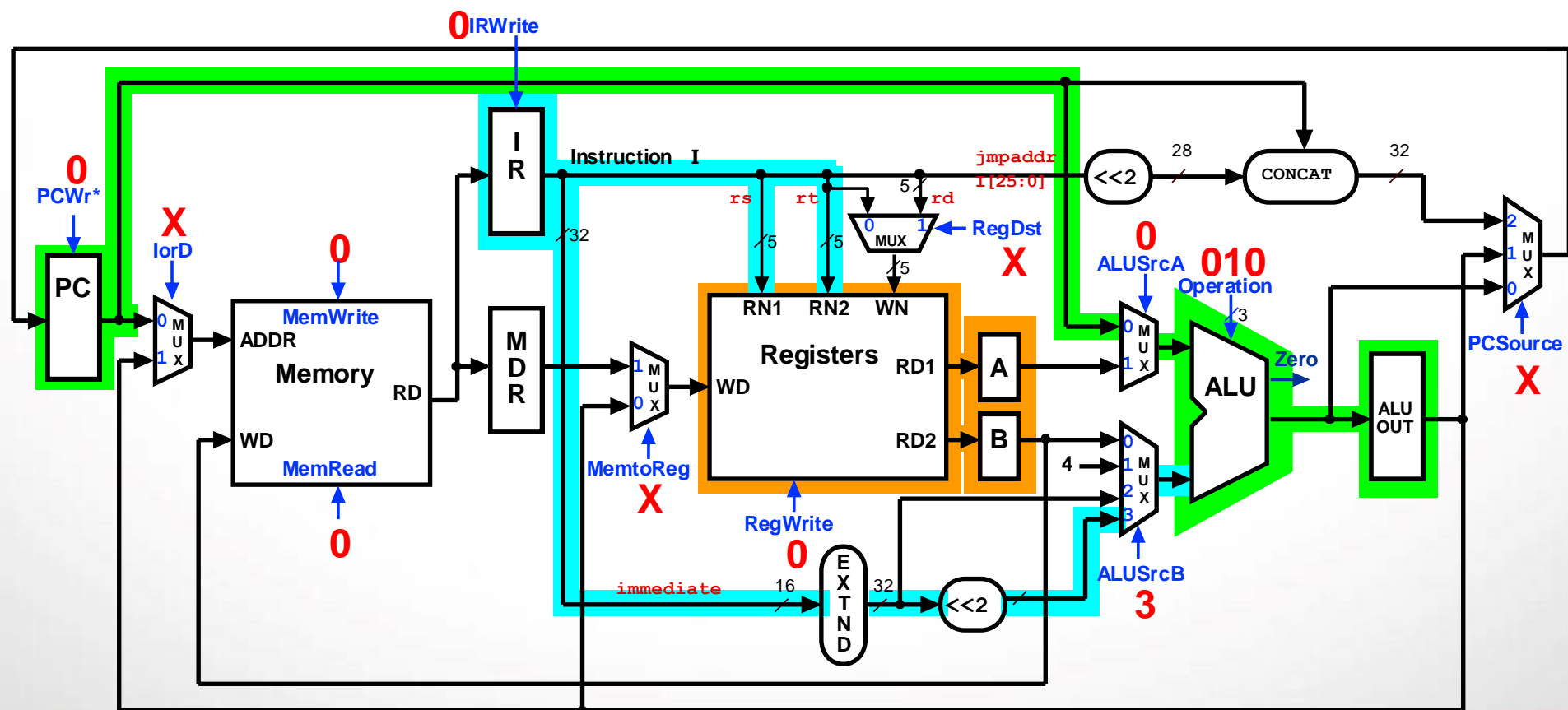
## 多周期执行步骤 (2):lw

```


A = Reg[IR[25-21]];          (A = Reg[rs])
B = Reg[IR[20-15]];          (B = Reg[rt])
ALUOut = (PC + sign-extend(IR[15-0]) << 2)
    
```





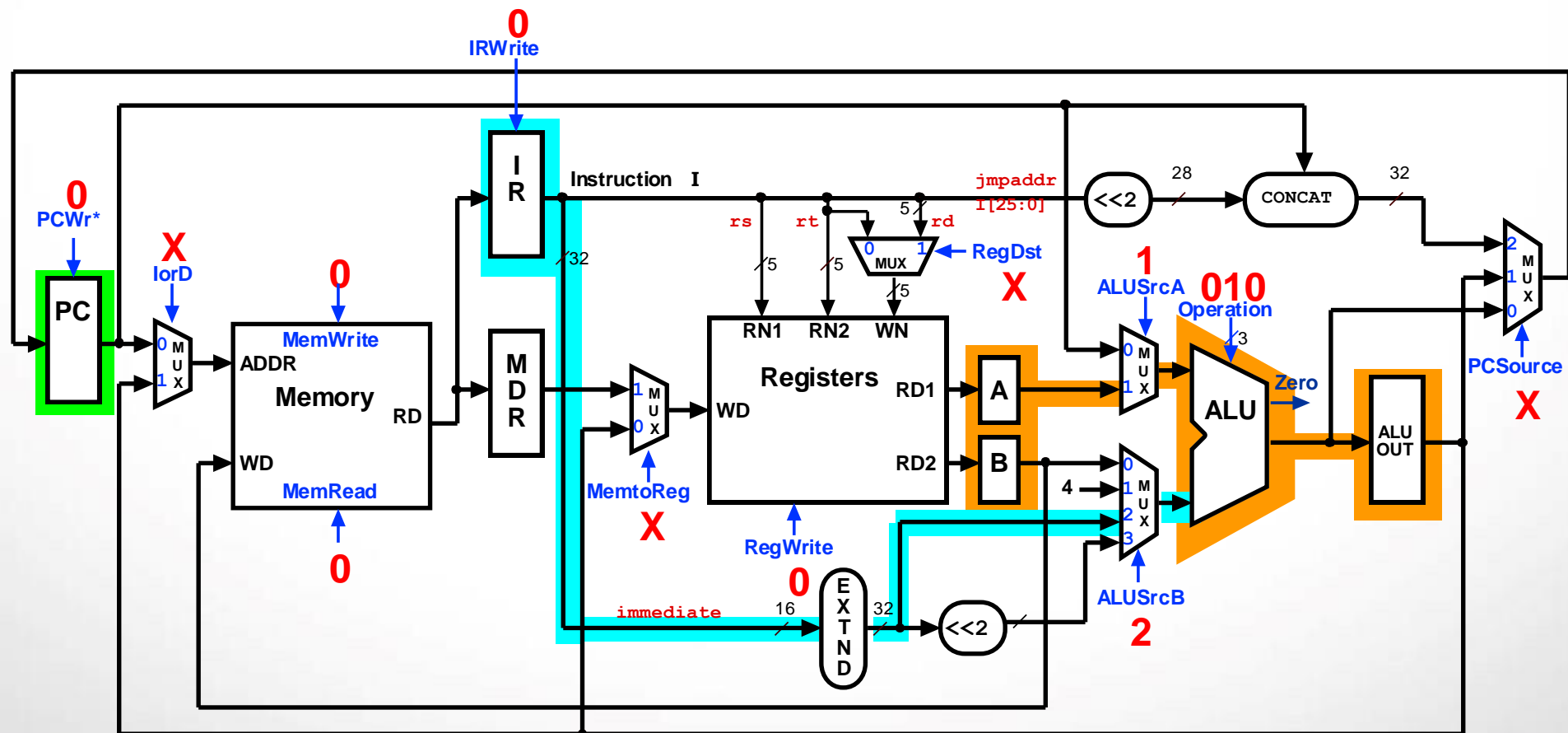
## 多周期执行步骤 (3):lw

$ALUOut = A + \text{sign-extend}(IR[15-0]);$




## 多周期执行步骤 (4) : lw

$MDR = Memory[ALUOut];$

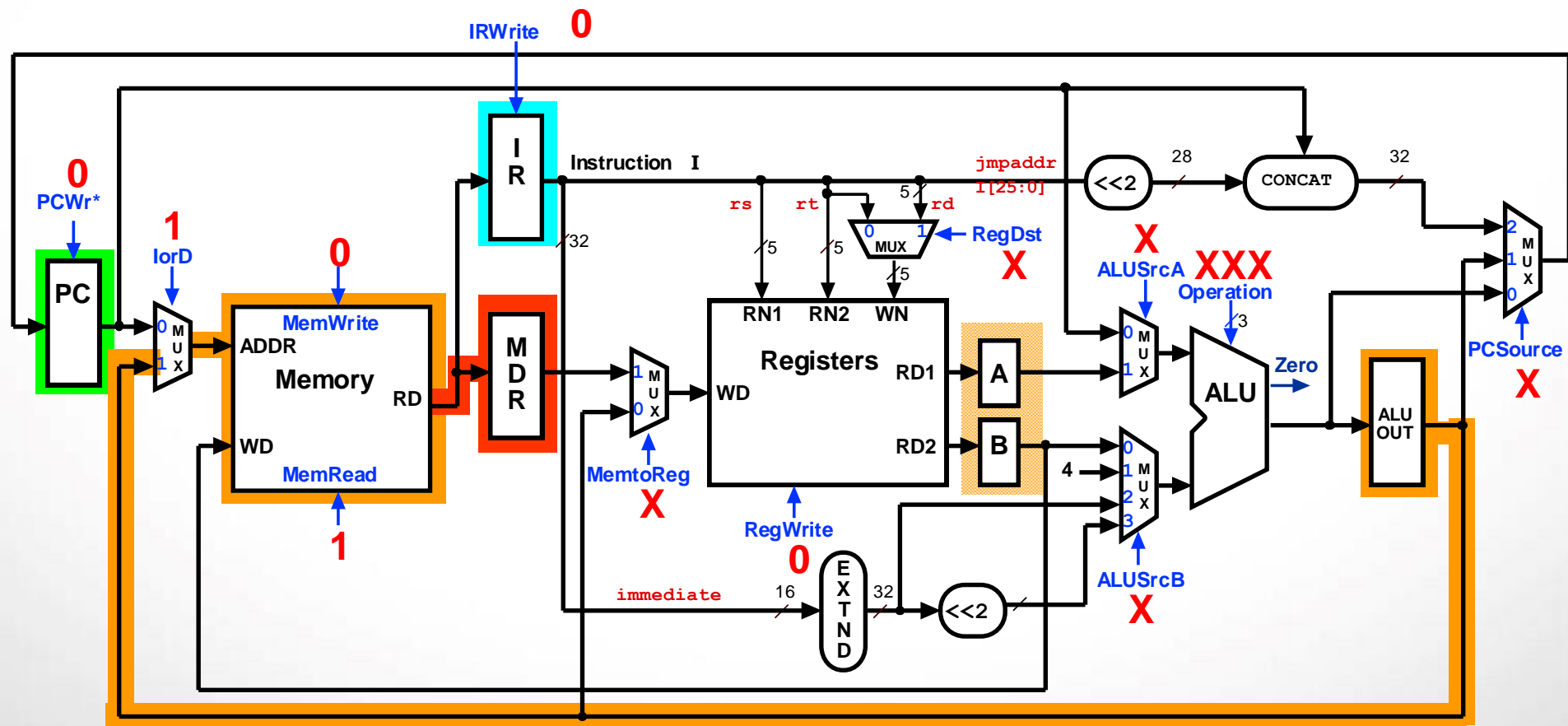
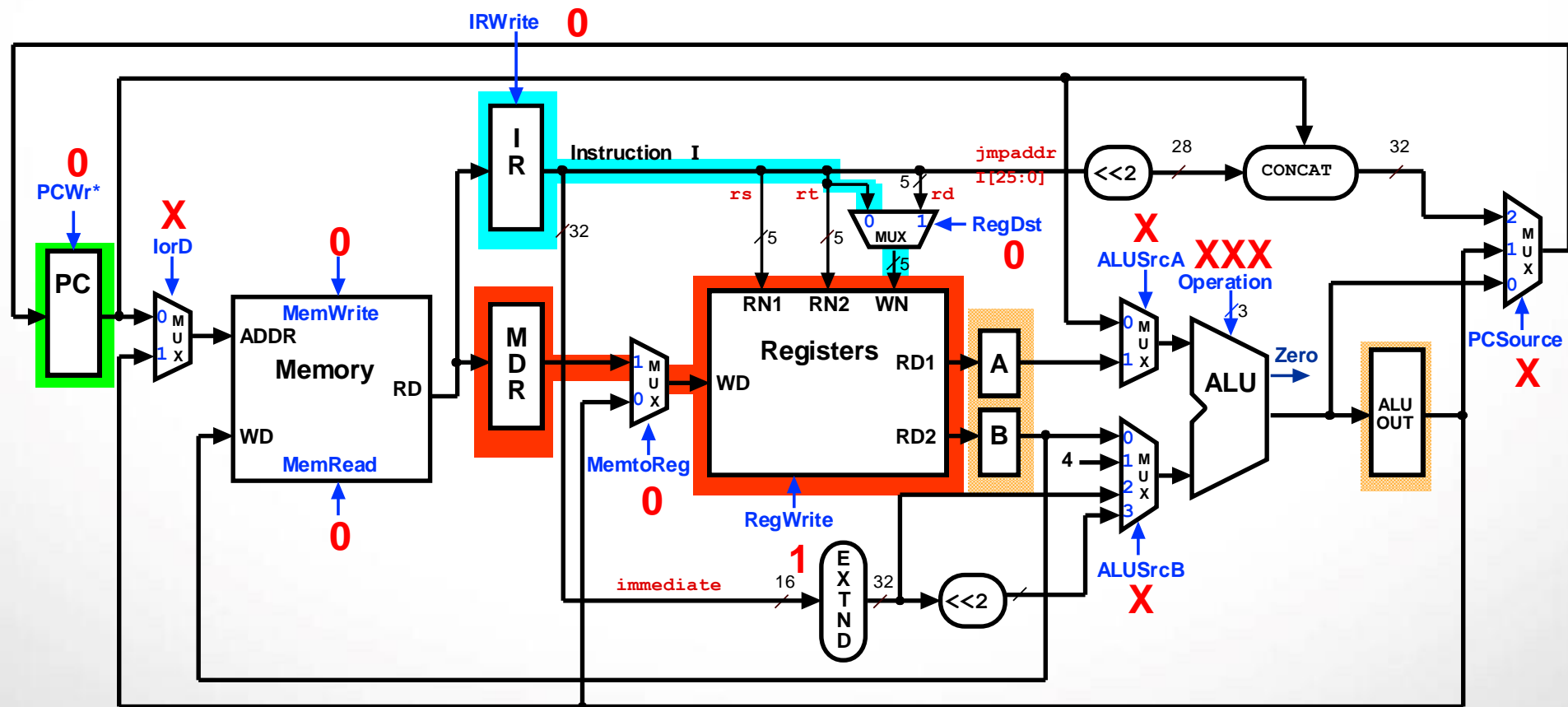
## 多周期执行步骤 (5) : lw


$\text{Reg}[\text{IR}[20-16]] = \text{MDR};$



# 多周期执行步骤 (1):sw

IR = Memory[PC];


PC = PC + 4;

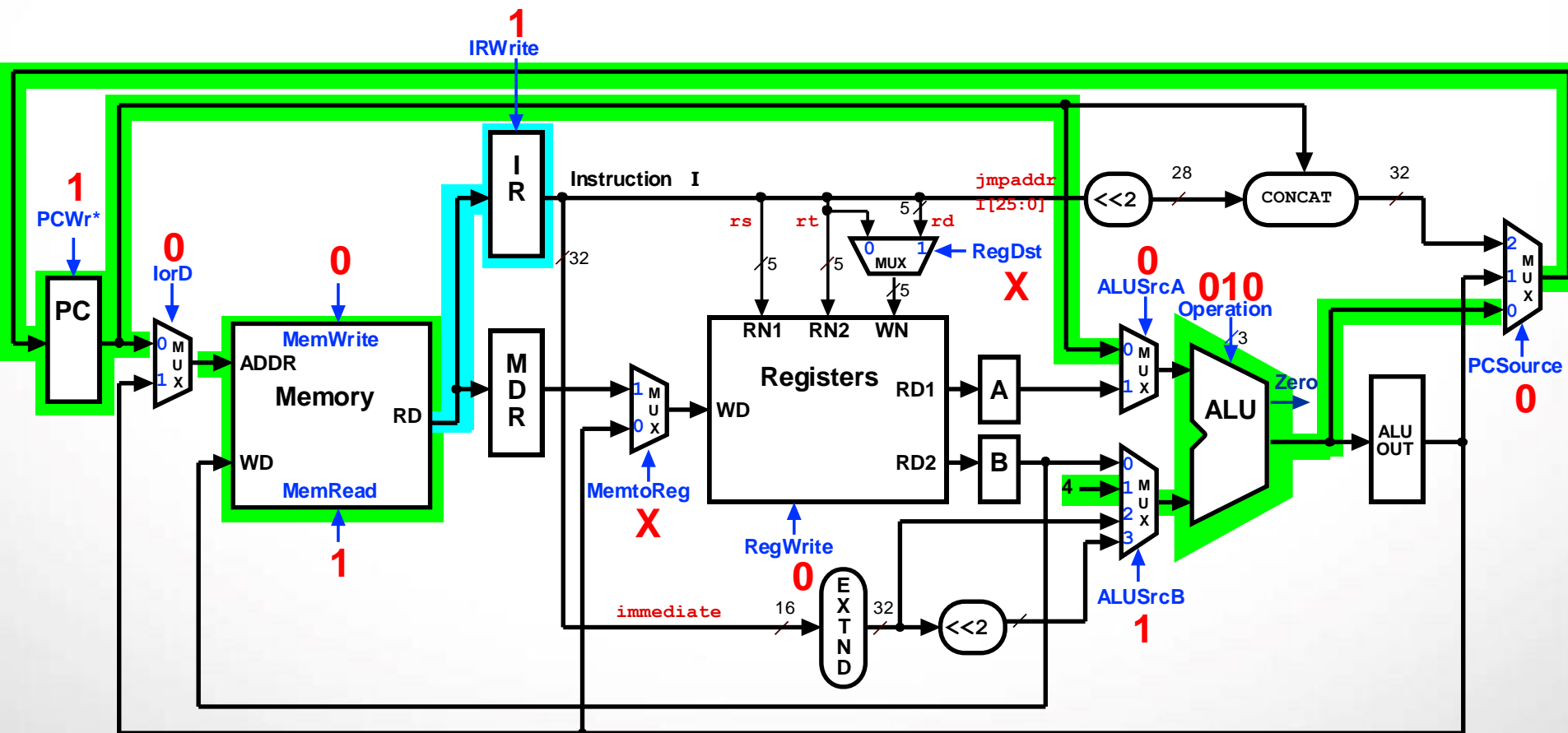
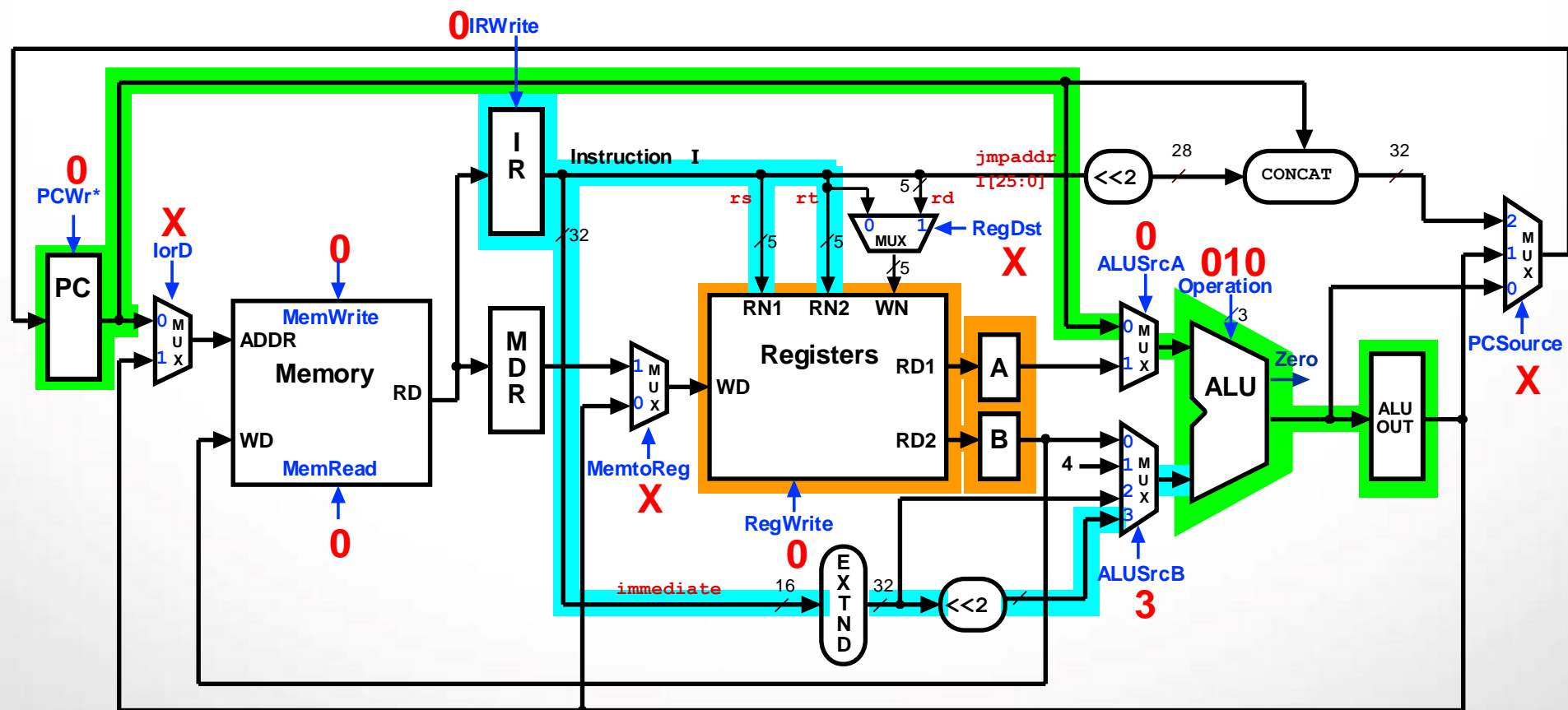
## 多周期执行步骤 (2):sw


```

A = Reg[IR[25-21]];          (A = Reg[rs])
B = Reg[IR[20-15]];          (B = Reg[rt])
ALUOut = (PC + sign-extend(IR[15-0]) << 2)
    
```



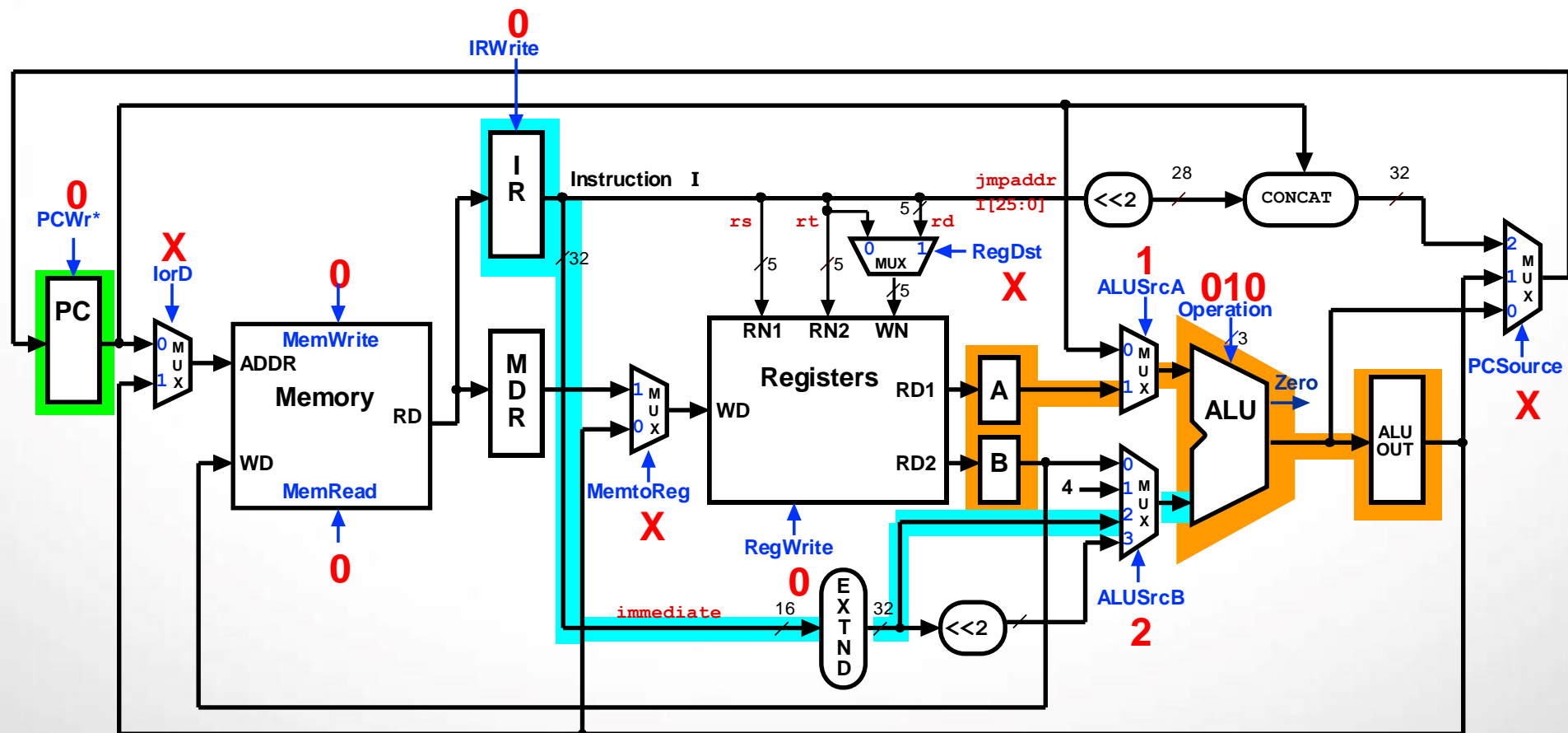
## 多周期执行步骤 (3):sw

$ALUOut = A + \text{sign-extend}(IR[15-0]);$



## 多周期执行步骤 (4) : SW


Memory[ALUOut] = B;

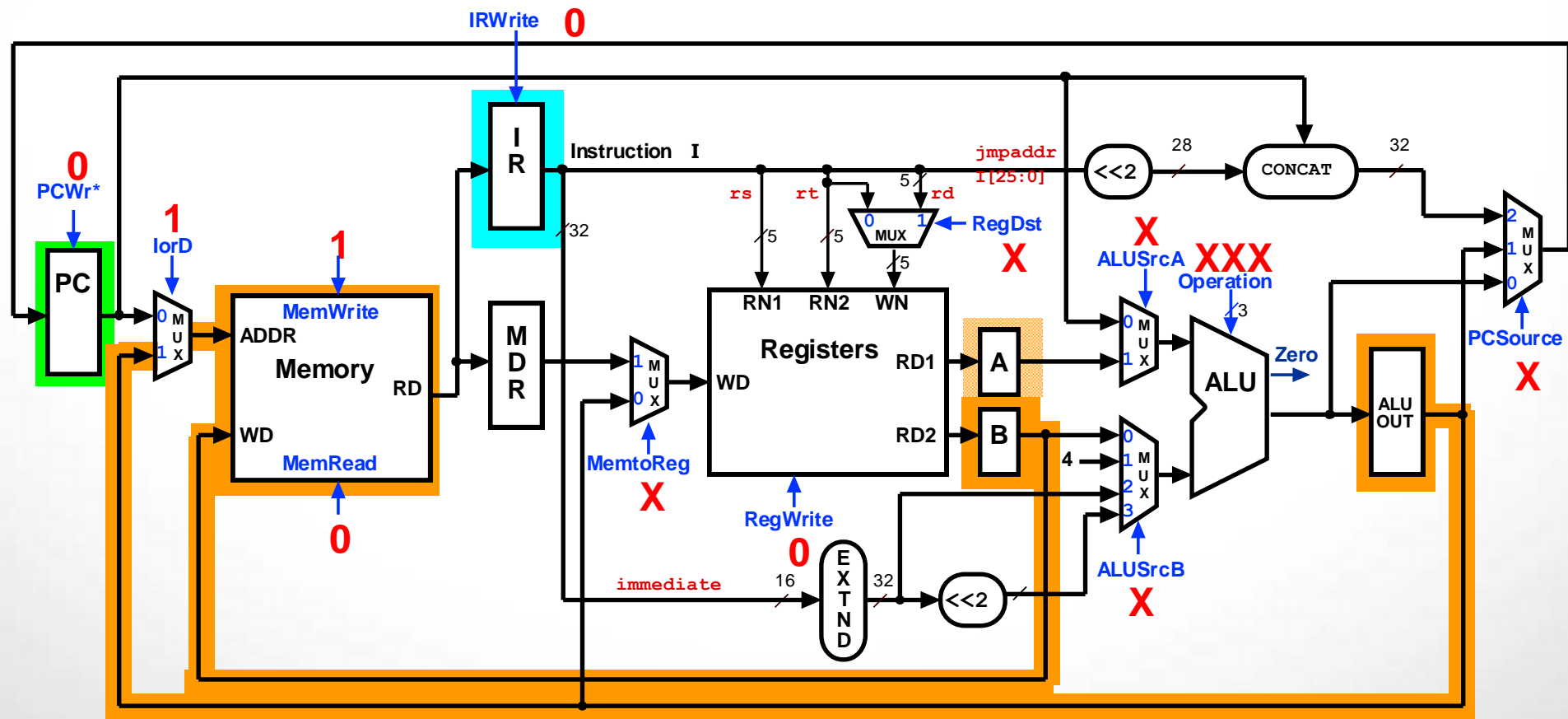

# 多周期执行步骤 (1) : Branch

IR = Memory[PC];

PC = PC + 4;

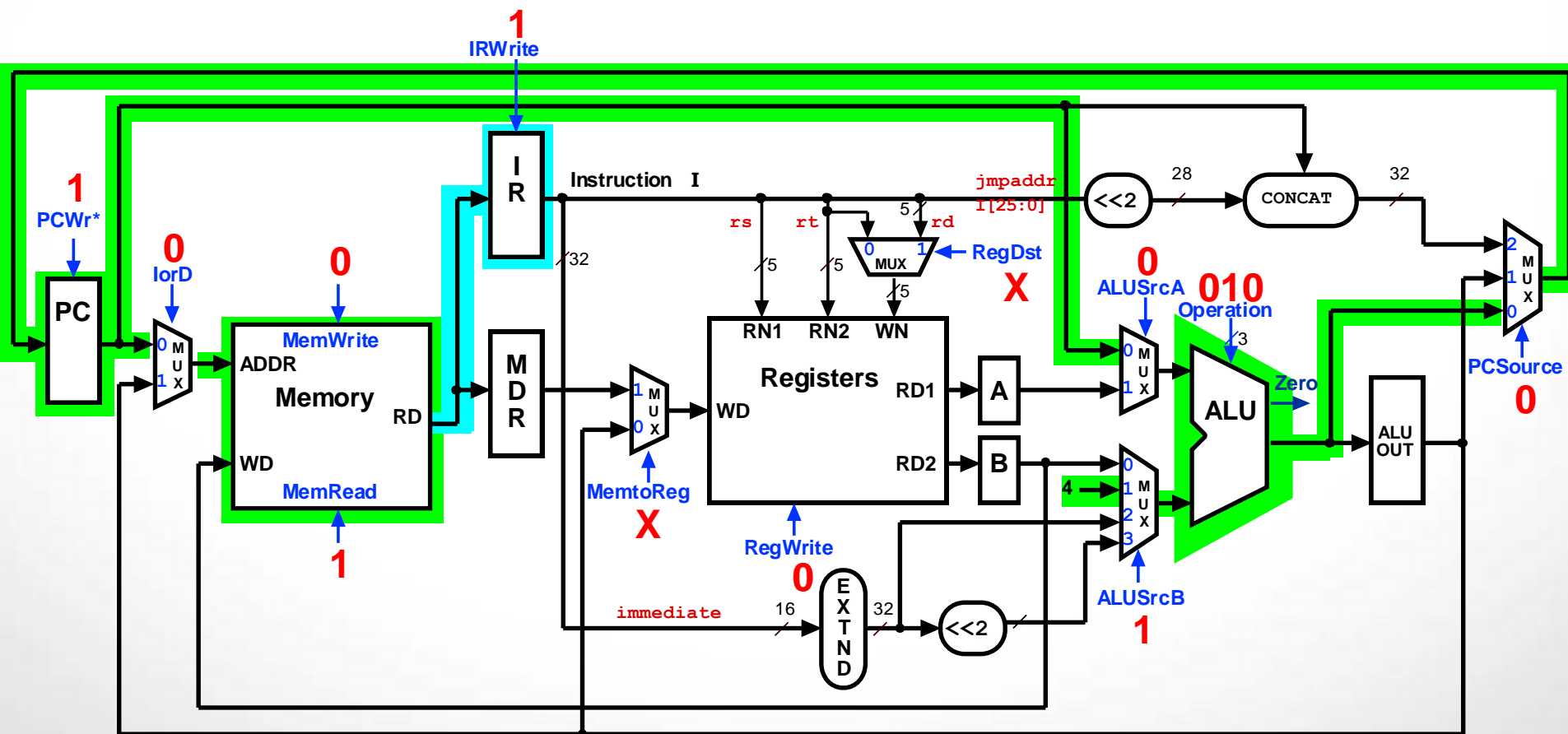



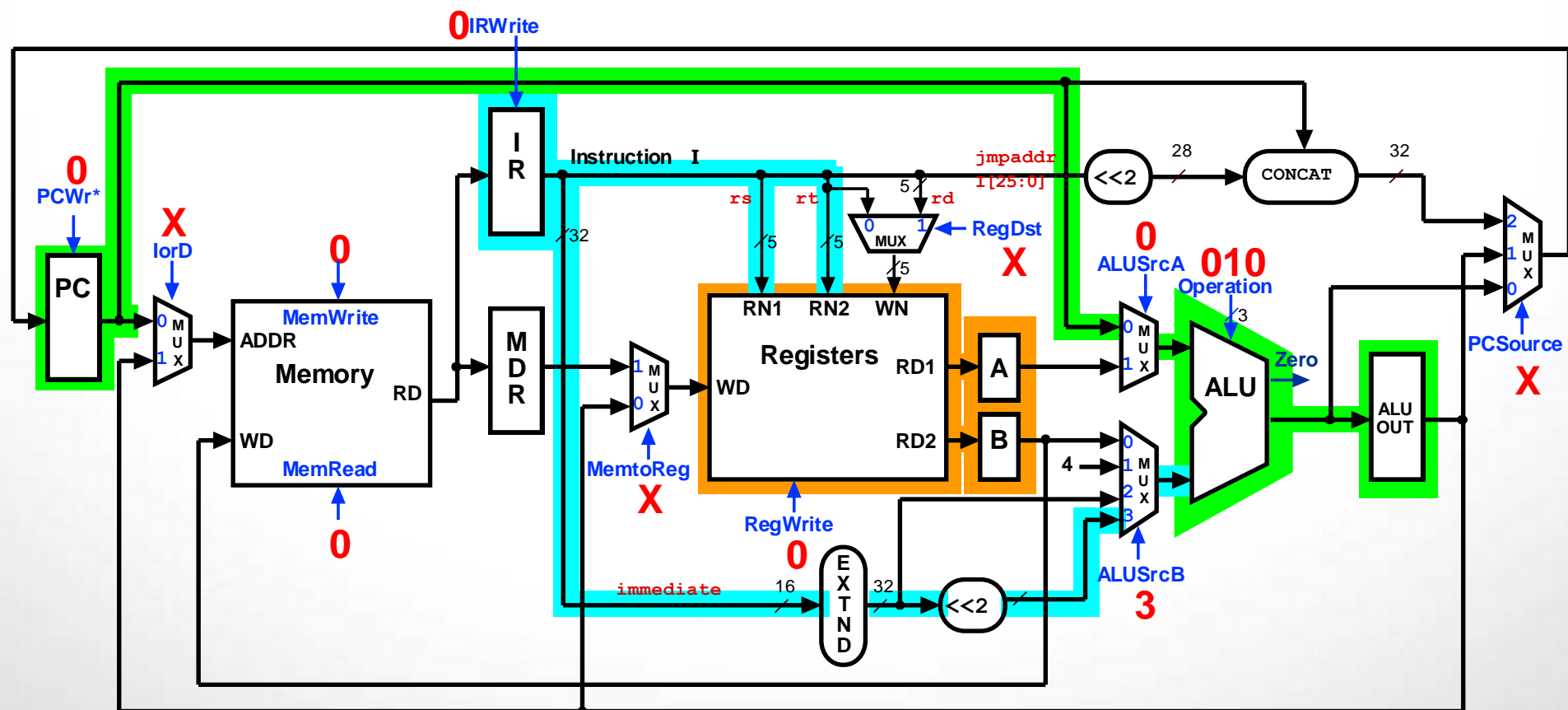
## 多周期执行步骤 (2) : Branch


```

A = Reg[IR[25-21]];           (A = Reg[rs])
B = Reg[IR[20-15]];           (B = Reg[rt])
ALUOut = (PC + sign-extend(IR[15-0]) << 2)
    
```



# 多周期执行步骤 (3) : Branch


if (A == B) PC = ALUOut;

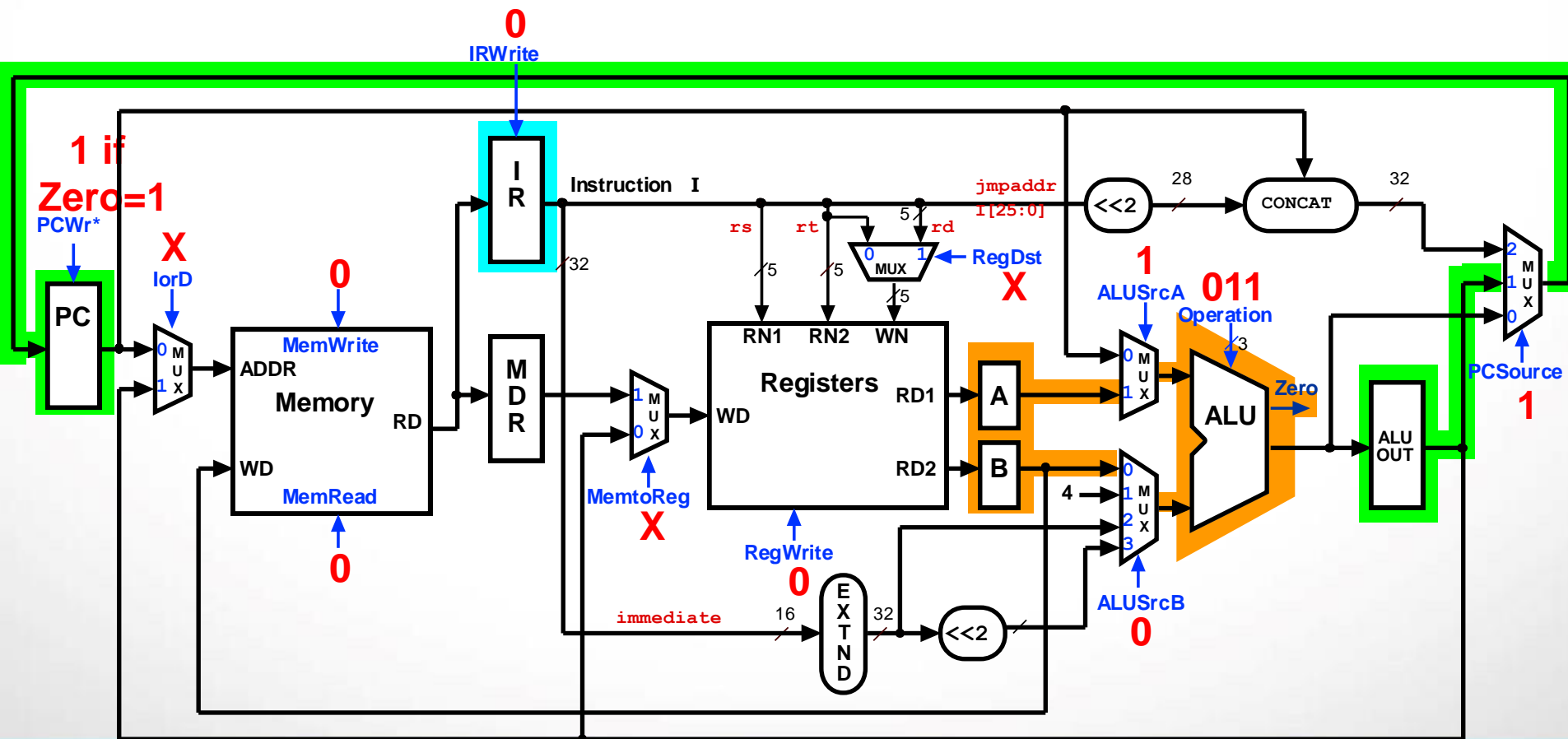

# 多周期执行步骤 (1) : Jump

IR = Memory[PC];


PC = PC + 4;

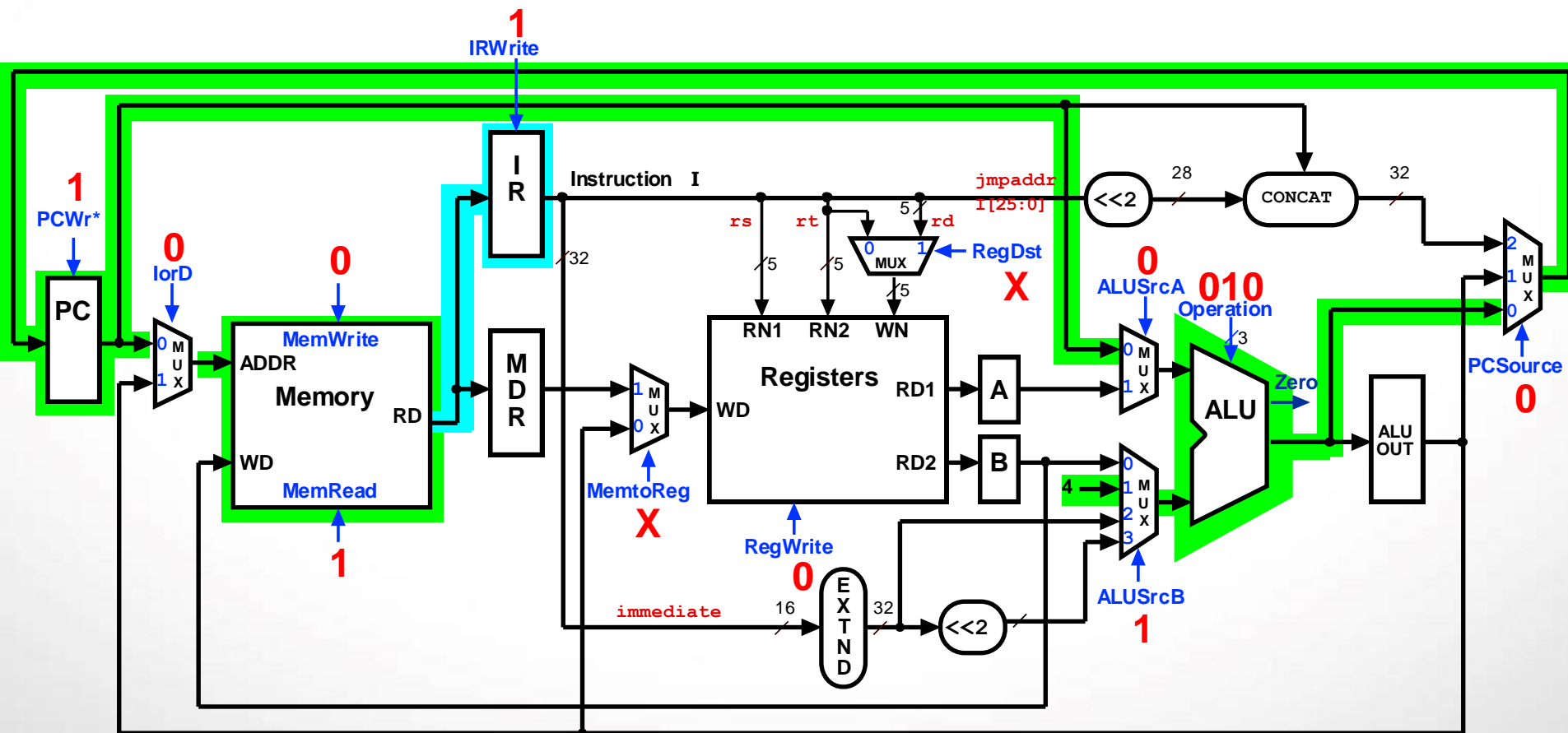
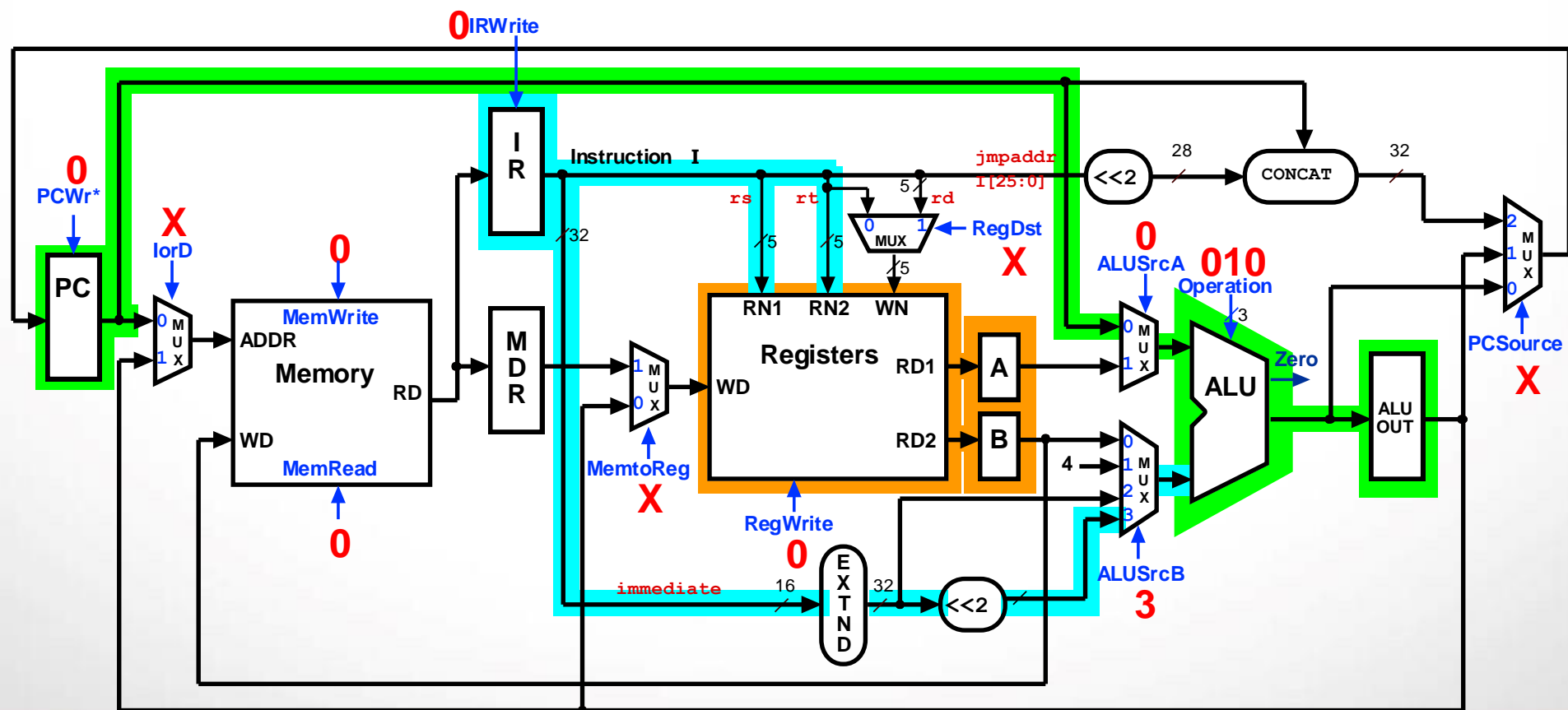
## 多周期执行步骤 (2) : Jump


```

A = Reg[IR[25-21]];          (A = Reg[rs])
B = Reg[IR[20-15]];          (B = Reg[rt])
ALUOut = (PC + sign-extend(IR[15-0]) << 2)
    
```


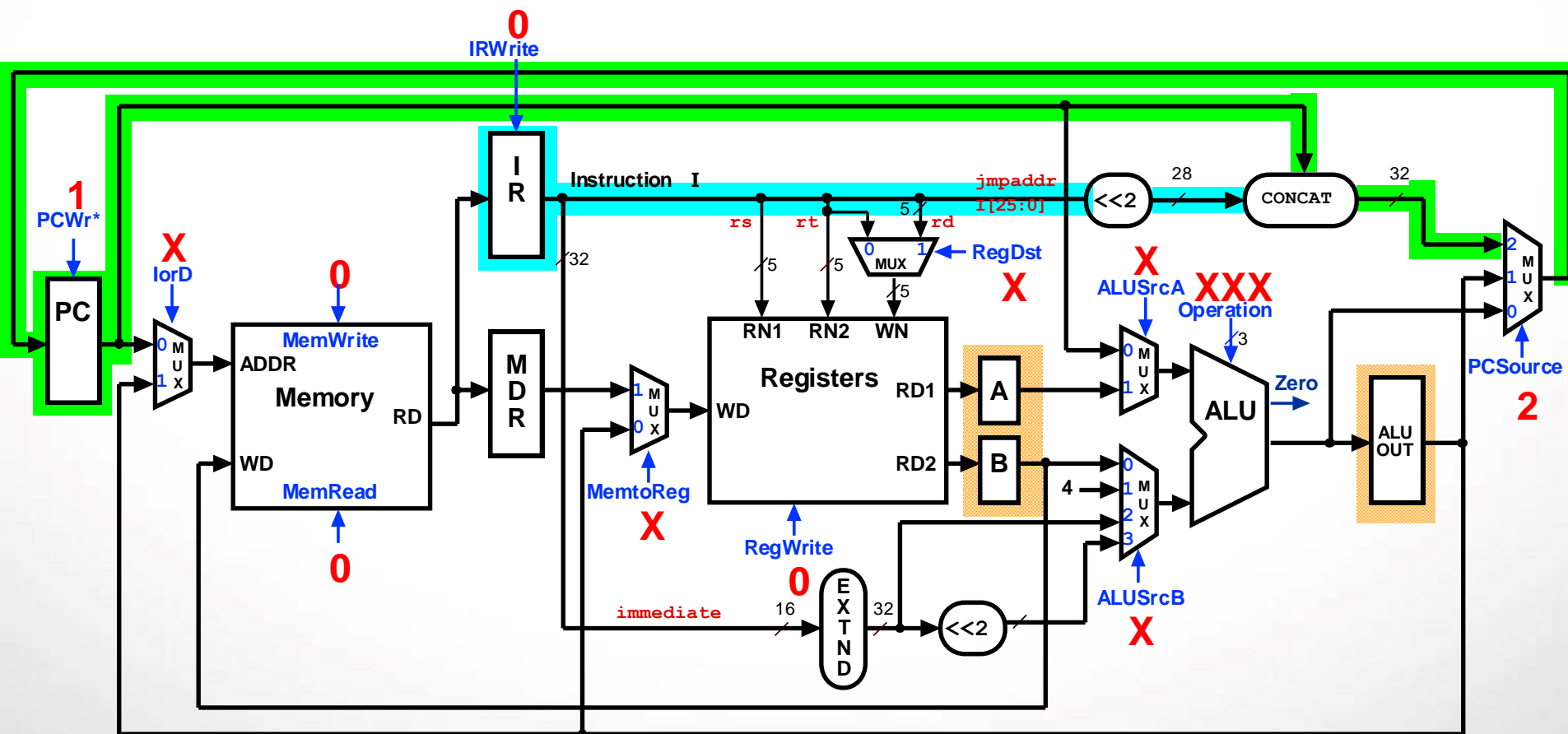
# 多周期执行步骤 (3) : Jump

$PC = PC[21-28] \text{ concat } (IR[25-0] \ll 2)$



# 完整数据通路 & 控制

